



# NORTH SOUTH UNIVERSITY

DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING

## EEE 111 / ETE 111 – Lab

Electronics - 1

Faculty : Dr. Riasat Khan  
Lab Instructor : Mehrab Hossain Likhon

### Lab Report

Experiment No : 04  
Experiment Name : Clipper and Clamper Circuits.

Date of Performance : 07-11-2021  
Date of Submission : 14-11-2021

Section:

Group No:

Group Member Info and Remarks:

Name	ID	Writer	Remarks
1. Md . Khalilur Rahman	1811835042	<input type="checkbox"/>	
2. Md. Raqibur Rahman Roni	1812935642	<input type="checkbox"/>	
3. Abdur Rahman Fahad	1912024642	<input type="checkbox"/>	
4. Md. Saeem Hossain Shanto	1912218642	<input checked="" type="checkbox"/>	

## Experiment Name: Clipper and Clamper Circuits.

### Abstract:

We studied the clipper and clamper circuits which gave us broad ideas about how they work and how they can modify the signals.

### Theory:

**Clipper:** The diode clipper also known as voltage limiter is a wave shaping circuit that takes an input waveform and clips or cuts off some portion of its input. Clippers remove signal voltage above and below a specified level. Half wave rectifier can also be called as a clipper circuit. Because it clipped off the negative half cycle of the input signal.

### Types of Clipper circuits:

Diode clipper circuits can be divided into 4 general types:

- ❖ Clipper circuit without bias – 1. Positive Clipper, 2. Negative Clipper
- ❖ Clipper circuit with bias – 1. Positive Clipper with bias, 2. Negative clipper with bias

There is also a combiner clipper circuit which has both positive and negative clipper together. A diode connected in series with the load can clipped off any half cycle of input depending on the orientation of the diode.

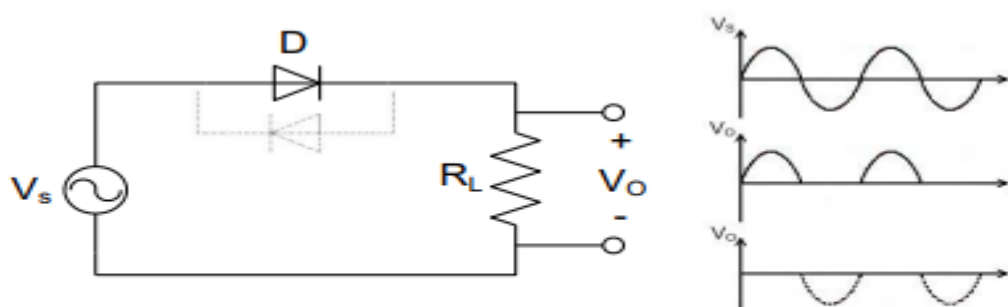


Figure 4.1: Simple Diode Clipper circuit

It is also possible to clip off a certain part of the input signal below a specified signal level by using a voltage source in reverse bias condition with the diode. If a battery of  $V$  volts is added to it, then for  $V_s$  above  $(V+0.7)$  volts the diode becomes forward bias and turns ON. The load receives above this voltage level.

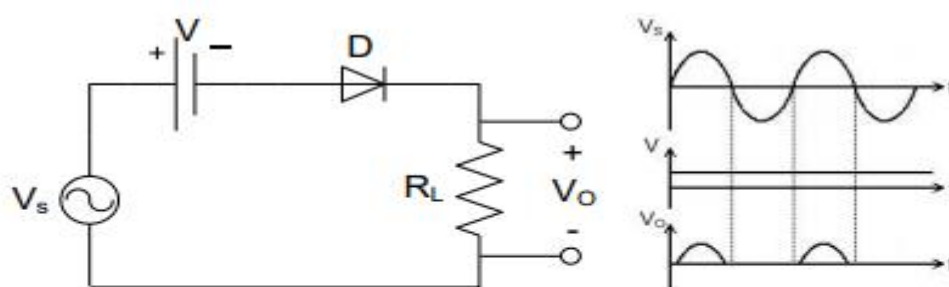


Figure 4.2: Clipper Circuit Using Bias Diode.

A diode connected in parallel with the load can clip off the input signal above 0.7 volts of one half cycle depending on the connection of the diode. Using two diodes in parallel in opposite direction both the half cycle can be limited to 0.7 volts.

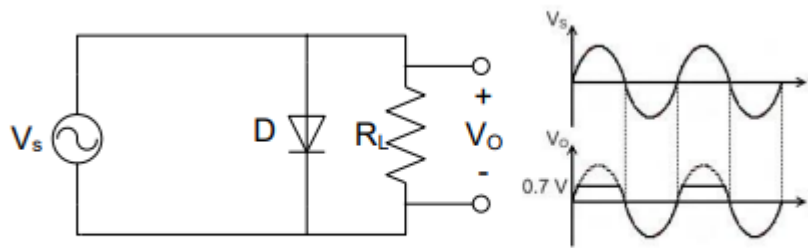


Figure 4.3: Parallel Clipper Circuit.

Using a biased Diode it is possible to limit the output voltage to a specified level depending on the attached battery voltage. Either the half cycles or both of them can be clipped off above a specified level.

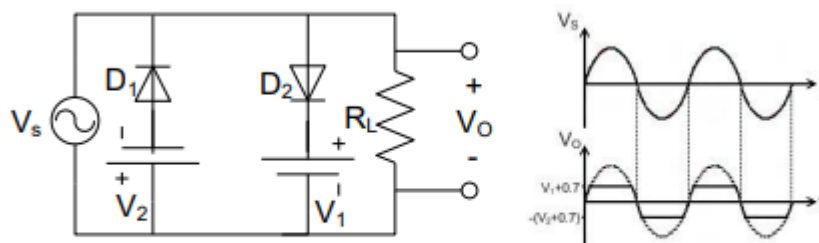


Figure 4.4: Biased Parallel Clipper Circuit.

In practical case for both the series and parallel clippers voltage source is not added. Required voltage levels are maintained by adding more semiconductor diode.

#### Applications of Clipper Circuit:

- Used in FM transmitters to reduce noise
- To limit the voltage input to a device
- To modify an existing waveform to the desired output

**Clamper:** A Clamper is an electric circuit that changes the DC level of the DC level of a signal to the desired level without changing the shape of the applied signal. In other words, the clamper circuit moves the whole signal up or down. A DC clamper circuit adds a DC voltage to the input signal. For instance, if the incoming signal varies from -10 volts to +10 volts, a positive DC clamper will produce an output that ideally swing from 0 volts to 20 volts and a negative clamper would produce an output between 0 volts to -20 volts.

#### Types of Clamper Circuit:

- ❖ Diode clamper circuits can be divided into 4 general types:
  - Clamper circuit without bias – 1. Positive clamper, 2. Negative clamper
  - Clamper circuit with bias – 1. Positive clamper with bias, 2. Negative clamper with bias


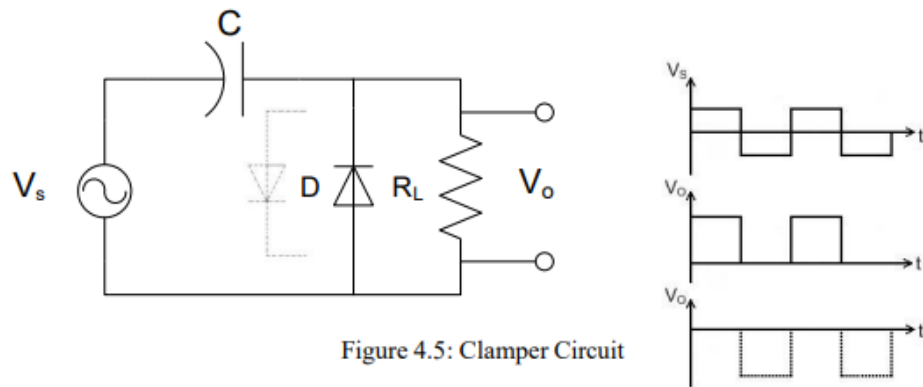



Figure 4.5: Clamper Circuit

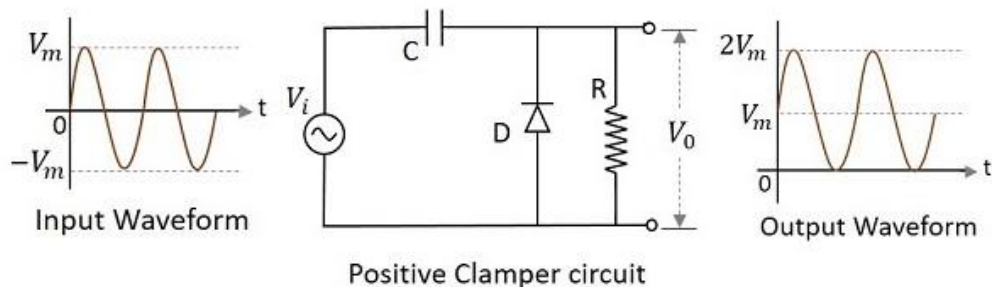A Positive Clamper circuit is one that consists of a diode, a resistor and a capacitor and that shifts the output signal to the positive portion of the input signal. The figure below explains the construction of a positive clamper circuit.




Initially when the input is given, the capacitor is not yet charged and the diode is reverse biased. The output is not considered at this point of time. During the negative half cycle, at the peak value, the capacitor gets charged with negative on one plate and positive on the other.

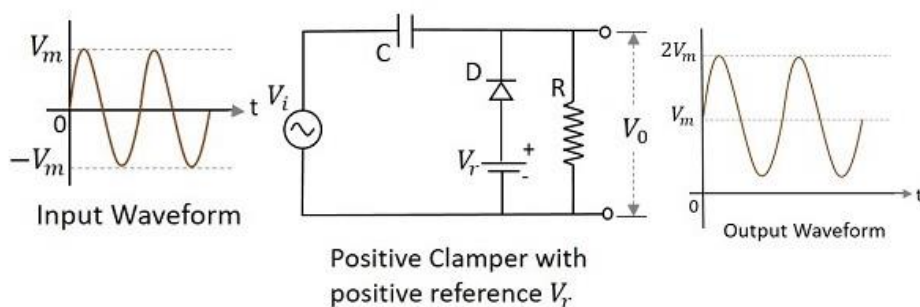
A Positive clamper circuit if biased with some positive reference voltage, that voltage will be added to the output to raise the clamped level. Using this, the circuit of the positive clamper with positive reference voltage is constructed as below.



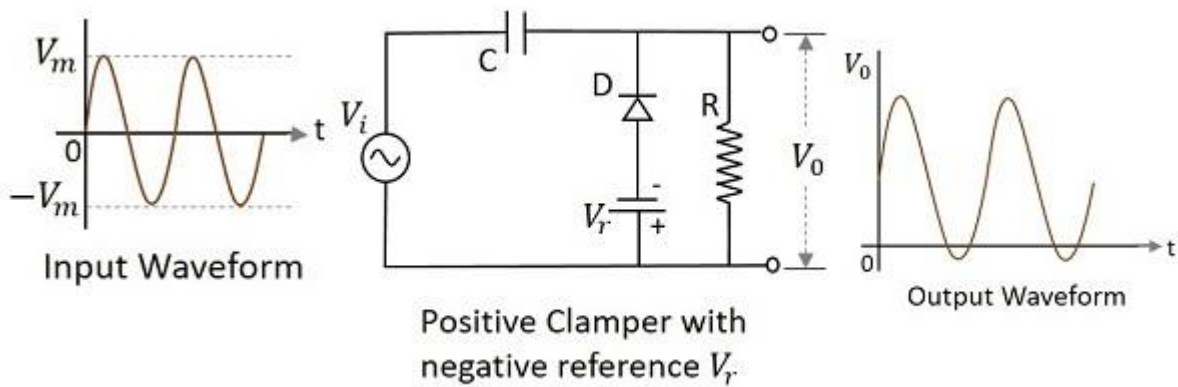A Positive clamper circuit if biased with some negative reference voltage, that voltage will be added to the output to raise the clamped level. Using this, the circuit of the positive clamper with positive reference voltage is constructed as below.




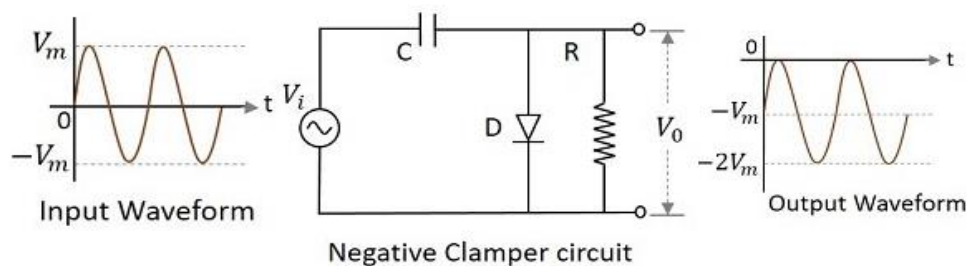On the other hand, a Negative Clamper circuit is one that consists of a diode, a resistor and a capacitor and that shifts the output signal to the negative portion of the input signal. The figure below explains the construction of a negative clamper circuit.




During the positive half cycle, the capacitor gets charged to its peak value  $V_m$ . The diode is forward biased and conducts. During the negative half cycle, the diode gets reverse biased and gets open circuited.

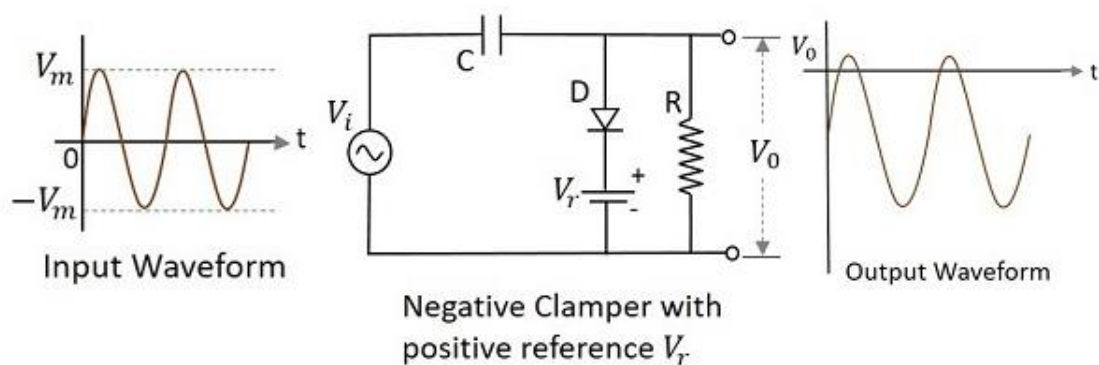A Negative clamper circuit if biased with some positive reference voltage, that voltage will be added to the output to raise the clamped level. Using this, the circuit of the negative clamper with positive reference voltage is constructed as below.



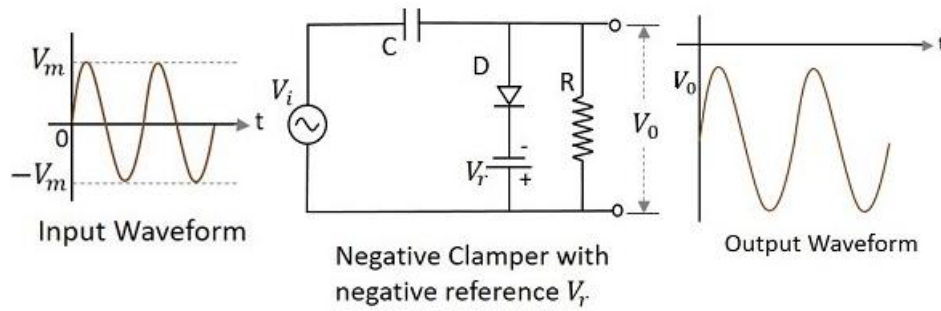A Negative clamper circuit if biased with some negative reference voltage, that voltage will be added to the output to raise the clamped level. Using this, the circuit of the negative clamper with negative reference voltage is constructed as below.



#### Applications of Clamper Circuit:

- Used as voltage doublers
- They find some applications in sonar and radar testing
- They are used to remove distortions in circuit
- Used in video processing equipment like TV

#### Equipment List:

Equipment Name	Value	Quantity
p-n junction diode	1N4007	1 piece
Resistor	100k $\Omega$	1 piece
Capacitor	0.1 $\mu$ F	1 piece
Signal		1 piece
Trainer Board		1 piece
DC Power Supply		1 piece
Oscilloscope		1 piece
Digital multi-meter		1 piece
Chords and wire		As required
Function Generator		1 piece


#### Circuit Diagram:

##### Series Clipper Circuit with bias:

1.


Md Saeem Hossain Shanto 1912218642

##### Series Negative Clipper

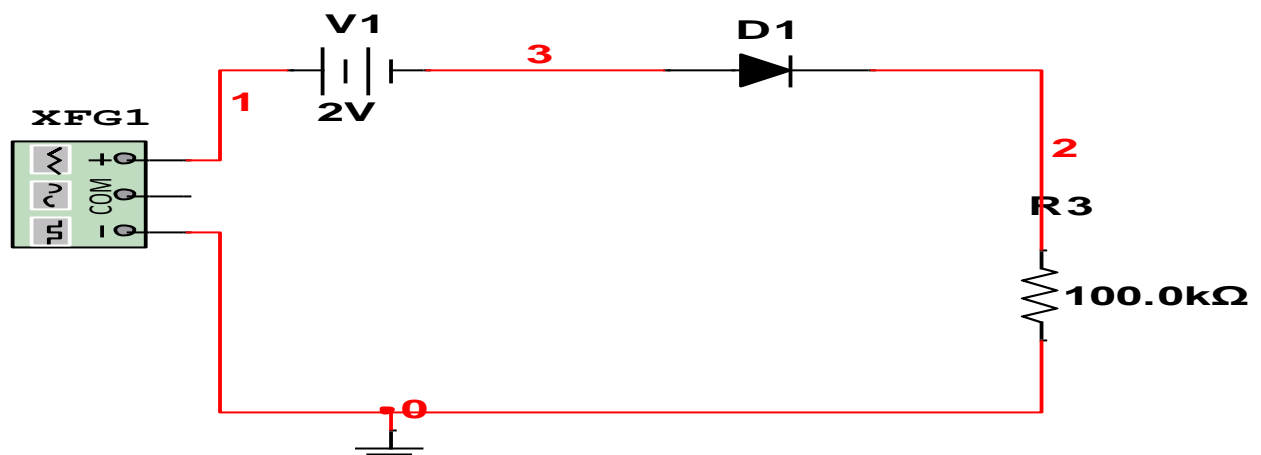

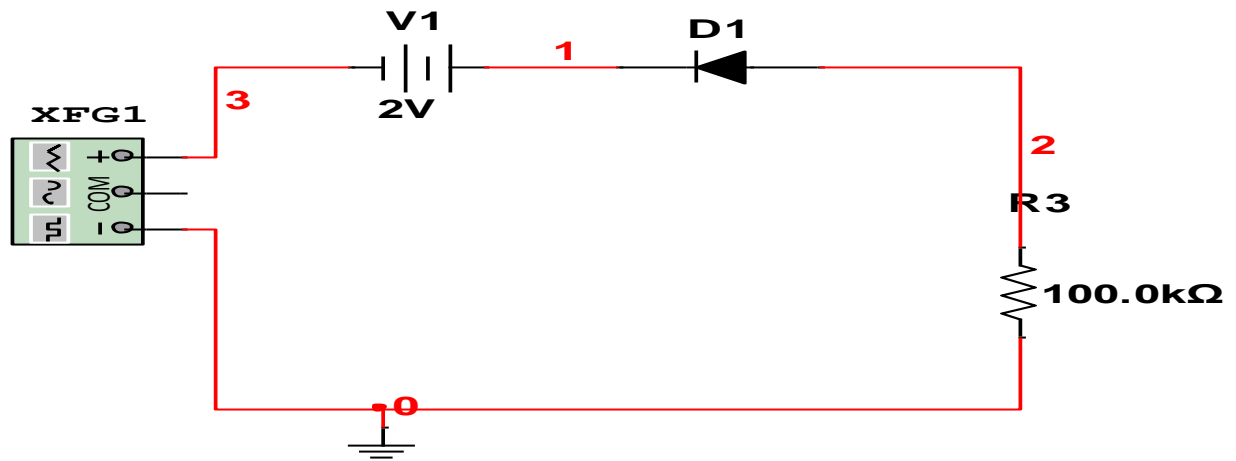2.


Md Saeem Hossain Shanto 1912218642  
Series Positive Clipper



Parallel Clipper Circuits with bias:

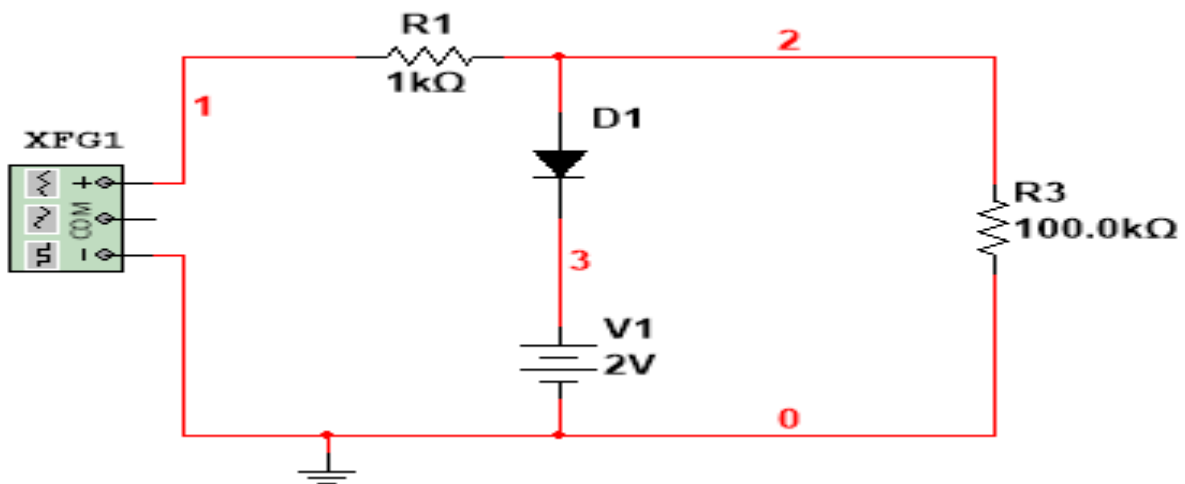1.


Md Saeem Hossain Shanto 1912218642  
Positive Clipper



2.

Md Saeem Hossain Shanto 1912218642

### Negative Clipper

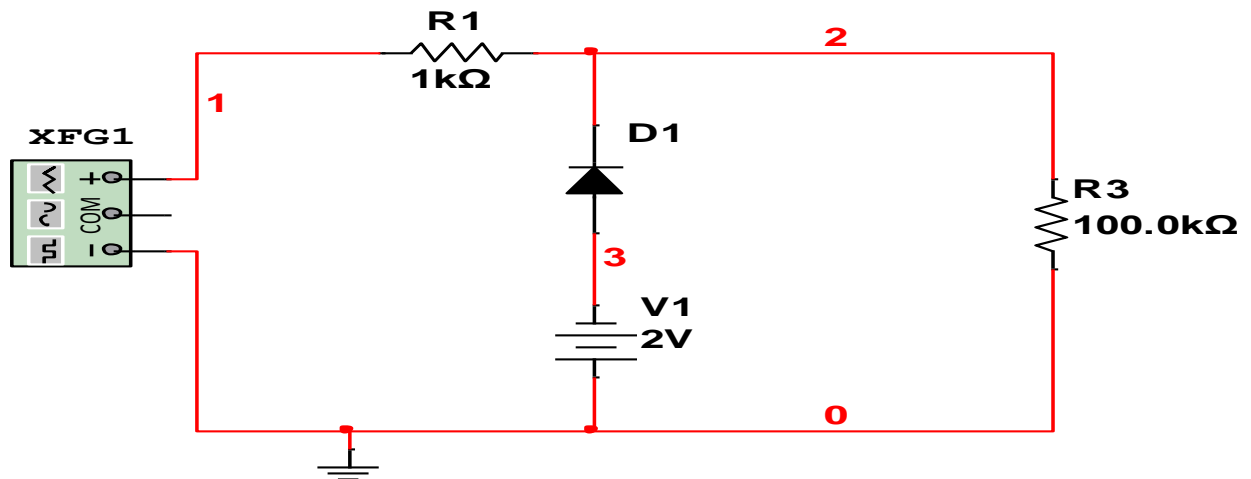

### Data Table:

Theoretical value:  $R = 1\text{k}\Omega$

Measured value:  $R = 1\text{k}\Omega$

$V_s = 5\text{ V(p-p)}$ .

$V_b$ (V)	$V_o$ (P-P)			
	Negative Clipper		Positive Clipper	
	$V_{\min}$	$V_{\max}$	$V_{\min}$	$V_{\max}$
0	-692.6453 mV	4.9505V	-4.9235V	692.4143m V
2	-2.6762V	4.9100V	-4.9235V	2.6766 V
5	-3.6610V	4.9100V	-4.9505V	3.6619 V

### Graphs:


Input voltage –  $2.5 V_p$




where  $V_{\max} = 4.9591\text{V}$ ,  $V_{\min} = -4.9727\text{V}$

### Negative Clipper with bias:


Bias voltage  $V_{\text{dc}}=0\text{V}$

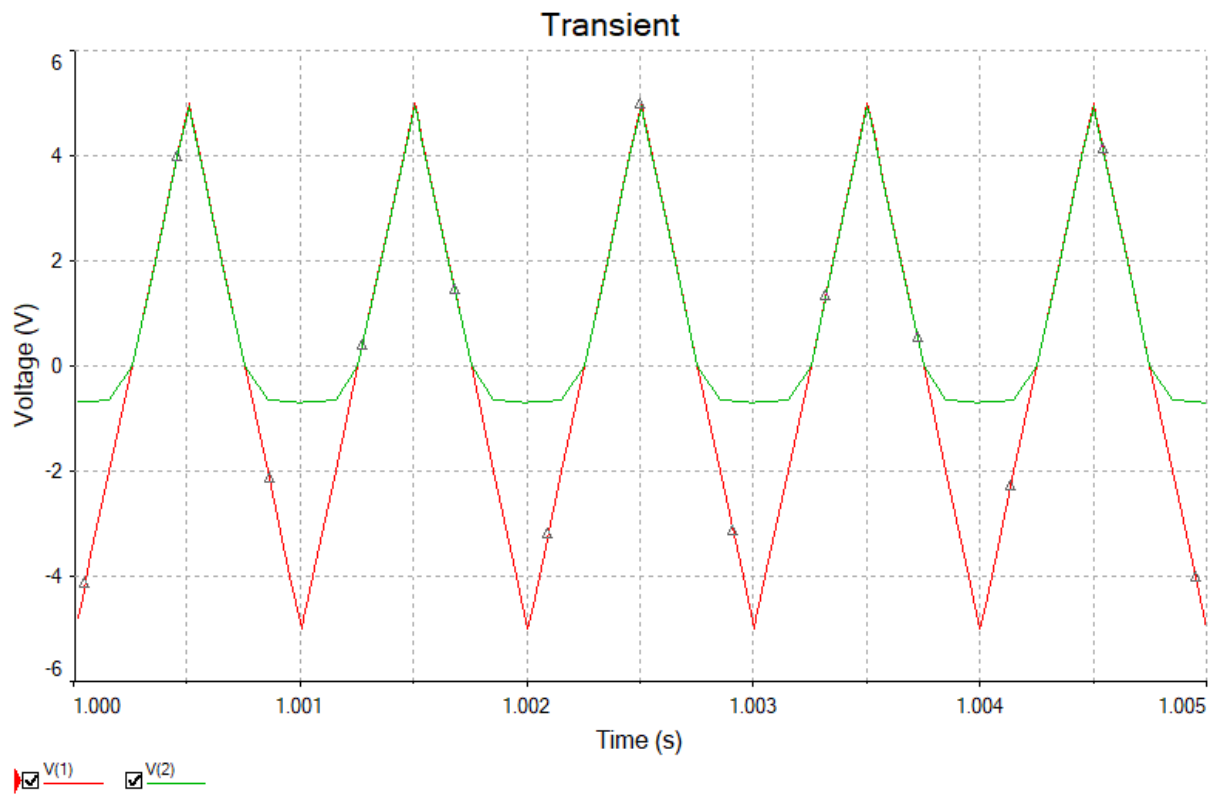


Bias voltage  $V_{\text{dc}}=2\text{V}$

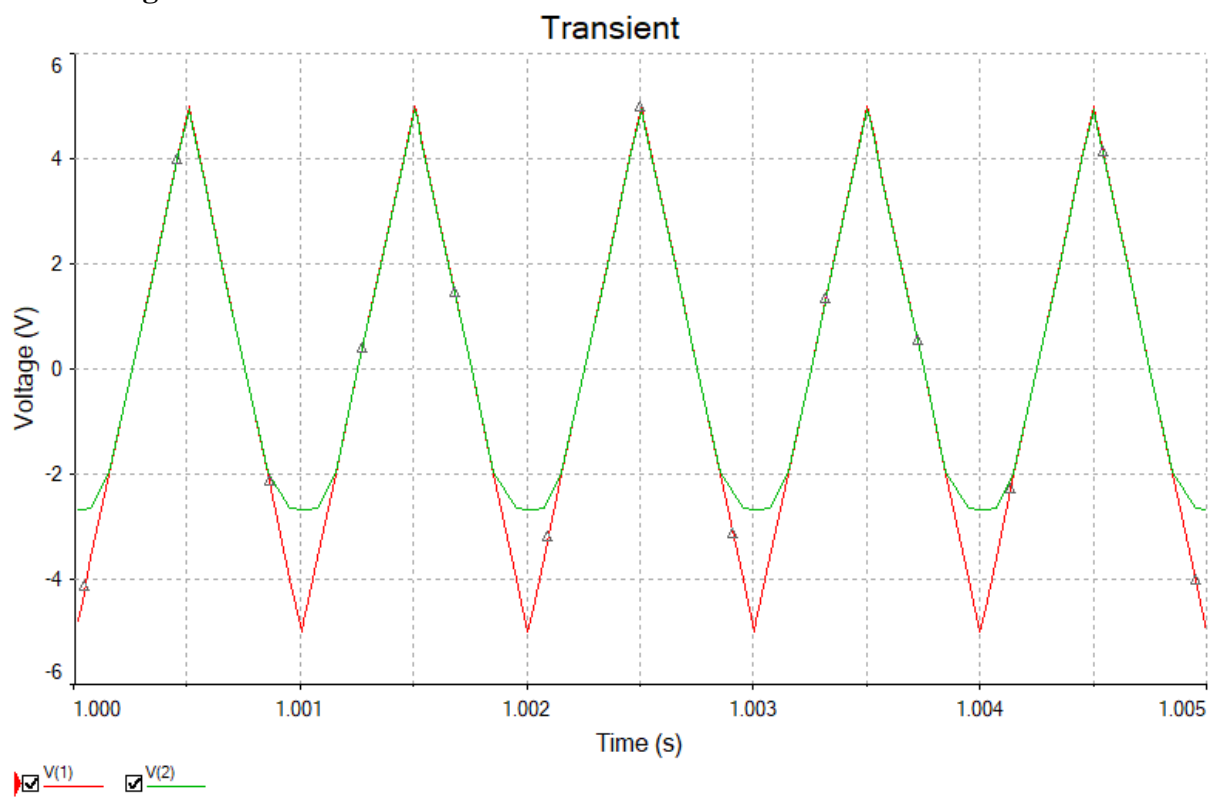


Bias voltage  $V_{\text{dc}}=3\text{V}$

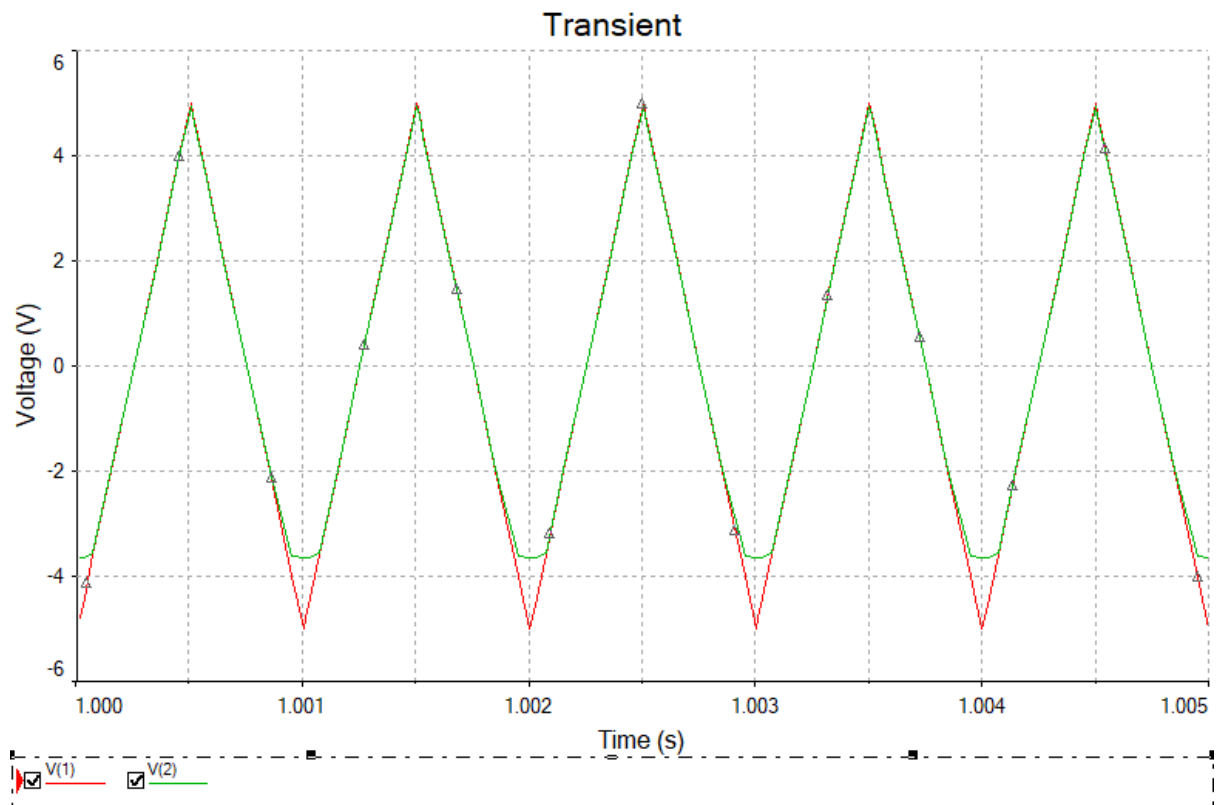

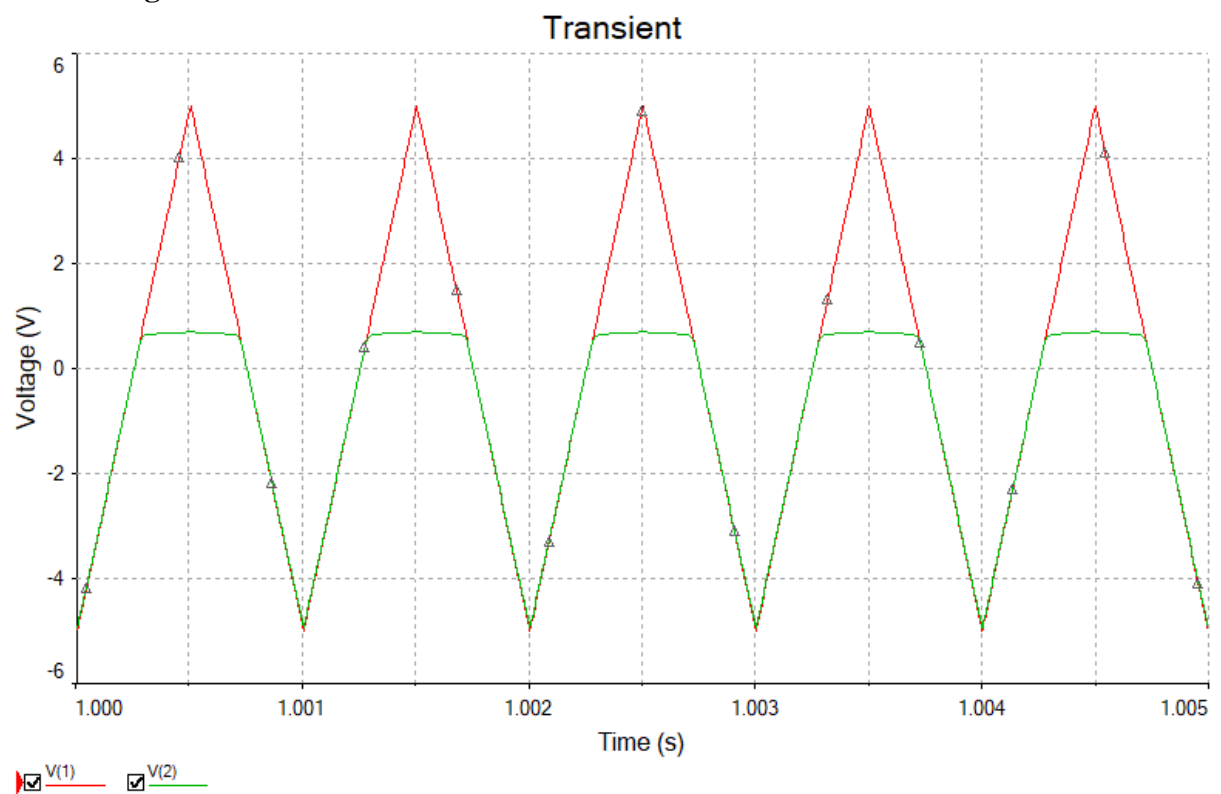
**Positive Clipper with bias:**  
**Bias voltage  $V_{dc}=0V$**



**Bias voltage  $V_{dc}=2V$**

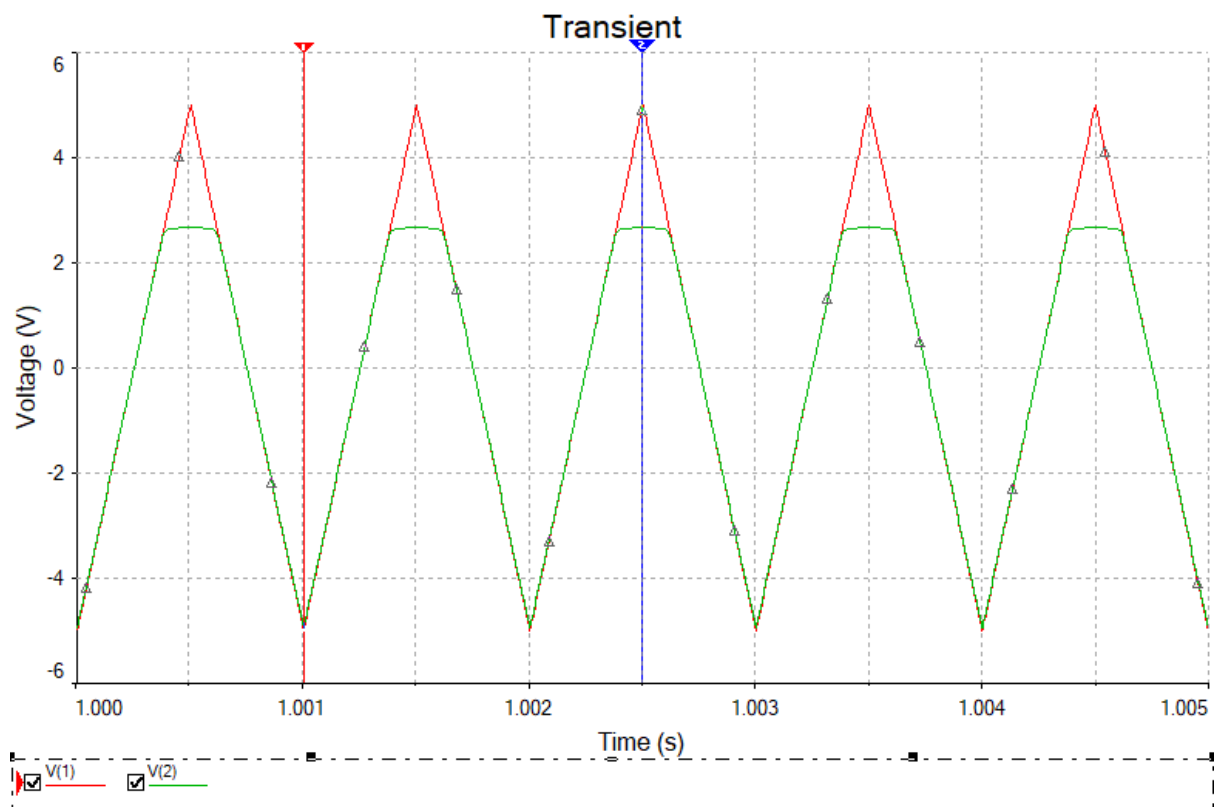

**Bias voltage Vdc=3V**

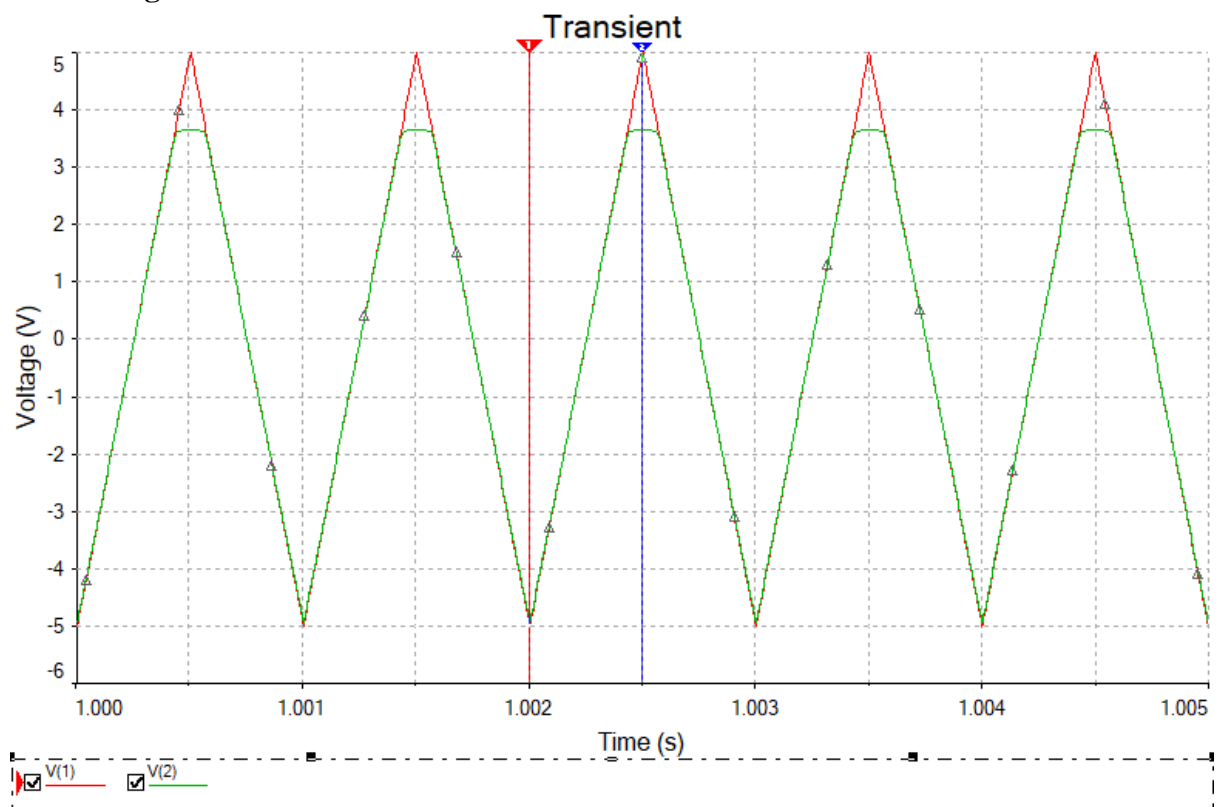

### **Result Analysis:**

From Negative clippers' graph, we can see that the negative clipper is cutting the negative signals of the output voltage. When the bias voltage was 0v , output  $V_{min}$  was -692.6453 mV, and when bias voltage was 2V output  $V_{min}$  was -2.6762V and when bias voltage was 3V, output voltage was -3.6610V . So we see that, the negative signal decreased as the bias voltage increased. But output  $V_{max}$  had no effect due to the negative clipper.

On the other hand, from Positive clipper's graph we see that the positive clipper is cutting the positive signals of the output voltage. When the bias voltage was 0v, output voltage  $V_{max}$  was 692.4143mV, when bias voltage was 2V, output voltage  $V_{max}$  was 2.6766 V and when bias voltage was 3V, output voltage  $V_{max}$  was 3.6619 V. The output voltage positive signal increased as we increased the bias voltage of the clipper. But the output voltage  $V_{min}$  had no effect by the positive clipper. It remained nearly constant all the time.

### **Conclusion:**

Using the negative clipper we can control the negative voltage signal flow of the circuit and positive clipper can be used to limit the positive voltage signal without affecting the other signals. As we see the negative clipper had no effect on the positive signal but it limited the negative signal flow of the output voltage from the negative clipper's output graph. The positive clipper does the same work with positive signal without effecting the negative signal. They does not distort the remaining part of the applied waveform.

### **References:**

1. **Electronic Devices and Circuit Theory, 11th Edition**

2. <https://www.circuitstoday.com/diode-clippers>

3.

[https://www.tutorialspoint.com/electronic\\_circuits/electronic\\_positive\\_clipper\\_circuits.html](https://www.tutorialspoint.com/electronic_circuits/electronic_positive_clipper_circuits.html)